




ENGINEERING DATA

VM630 Applications

3-Input x 1-Outputs Signal Combiner

The VM630 series of transformers may be wired in several ways to meet various needs and application requirements.

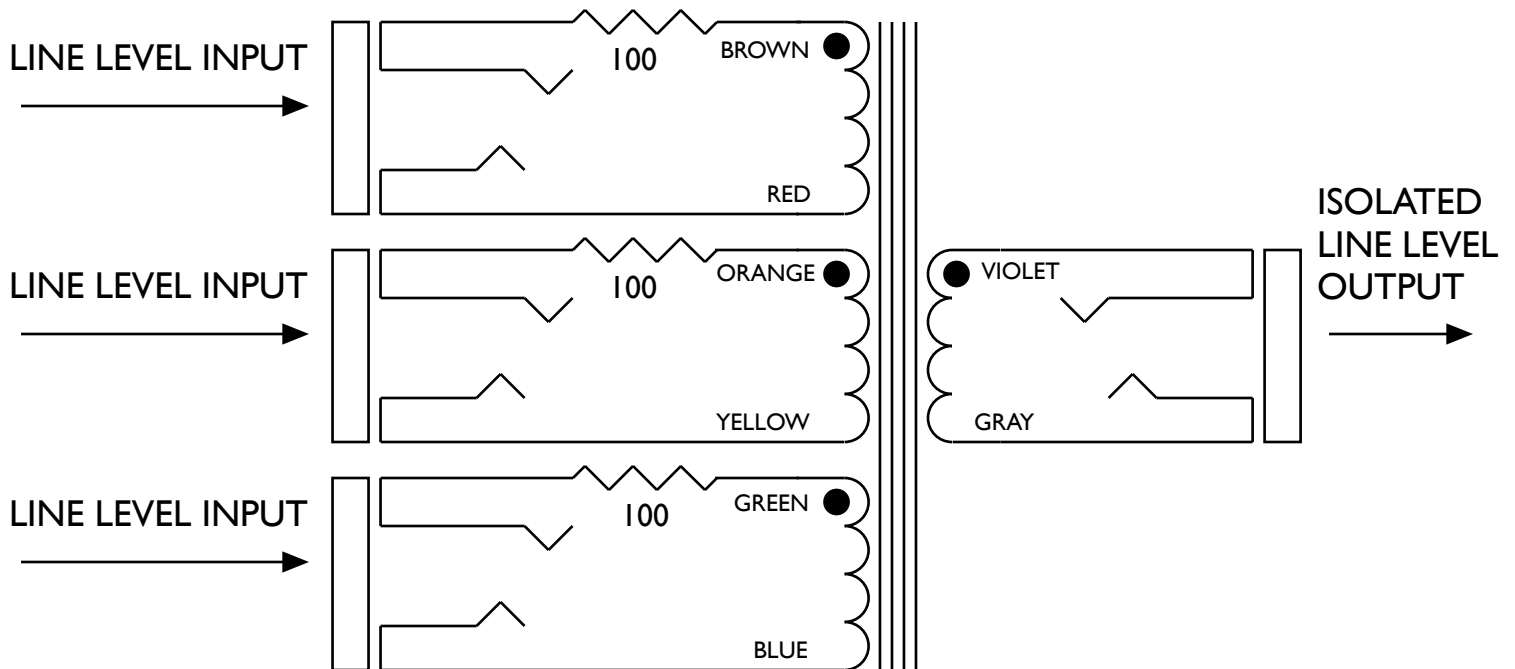In the schematic shown below the ratio from each line-level input to the line-level output is a little bit less than 1:1 due to insertion loss and the 100 ohm resistors in series with the inputs. DC currents should be blocked from entering the transformer.



The application shown has been tested and works, however, it is provided for use, strictly at your own risk. Layered Audio shall not be held liable for damages resulting from the use or misuse of products and information.